


Combinational - Assignment

- 1 Implement the following functions using
- 2:1 MUX and NOT gates
 - 4:1 MUX


$$\begin{aligned} \text{a) } F(A, B, C) &= \bar{A}C + B\bar{C} \\ &= \bar{A}C(B + \bar{B}) + (A + \bar{A})B\bar{C} \\ &= \bar{A}BC + \bar{A}\bar{B}C + AB\bar{C} + \bar{A}B\bar{C} \\ &= m(1, 2, 3, 6) \end{aligned}$$

TT (using 2:1 mux and not gates)

A	B	C	Y (output)	A	B	Y
0	0	0	0	0	0	0
0	0	1	1	0	1	1
0	1	0	1	1	0	0
0	1	1	1	1	1	0
1	0	0	0			
1	0	1	0			
1	1	0	1			
1	1	1	0			

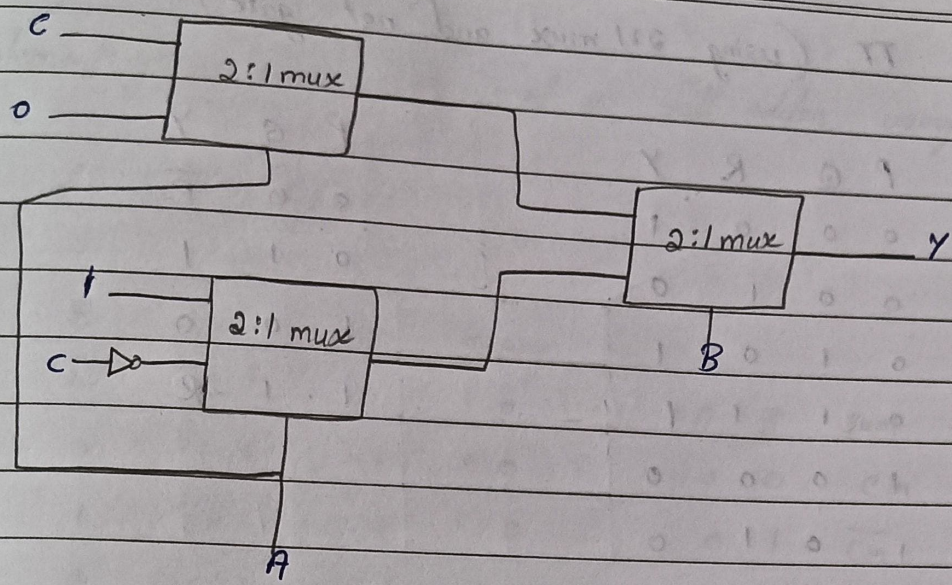

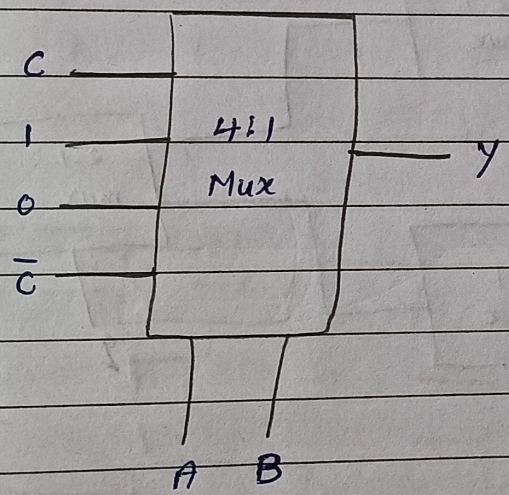ii) using 4:1 mux (follow the above truth table)




$$\begin{aligned}
 b) \quad F(P, Q, R) &= \bar{P}\bar{R} + Q\bar{R} + \bar{P}Q \\
 &= \bar{P}\bar{R}(Q + \bar{Q}) + (R + \bar{P})Q\bar{R} + \bar{P}Q(R + \bar{R}) \\
 &= \bar{P}Q\bar{R} + \bar{P}\bar{Q}\bar{R} + PQ\bar{R} + \bar{P}Q\bar{R} + \bar{P}QR + \bar{P}Q\bar{R} \\
 &= \bar{P}Q\bar{R} + \bar{P}\bar{Q}\bar{R} + PQ\bar{R} + \bar{P}QR
 \end{aligned}$$

$$y = \underline{m(0, 2, 4, 6)}$$


TT (using 2:1 mux and not gate)

P	Q	R	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

P	Q	Y
0	0	$\bar{R}$
0	1	1
1	0	0
1	1	$\bar{R}$

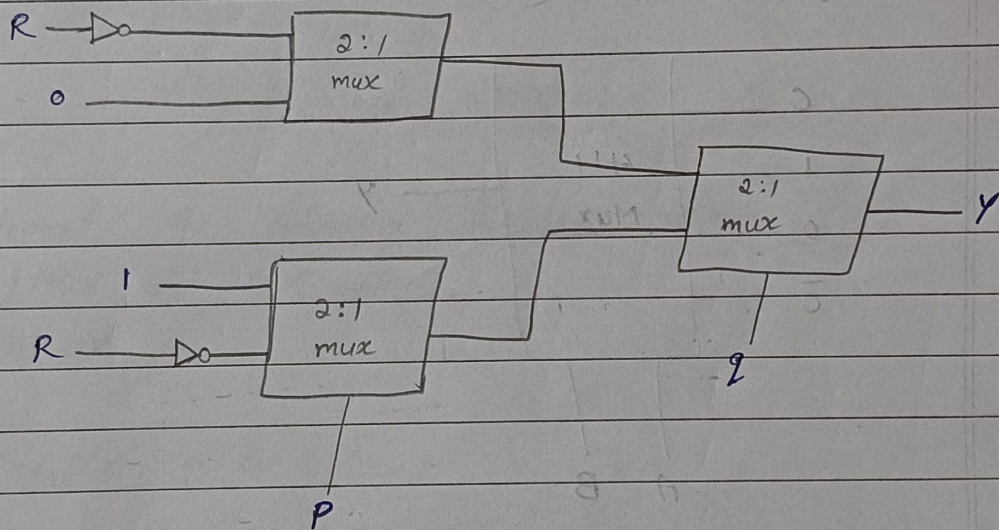



ii) using 4:1 mux

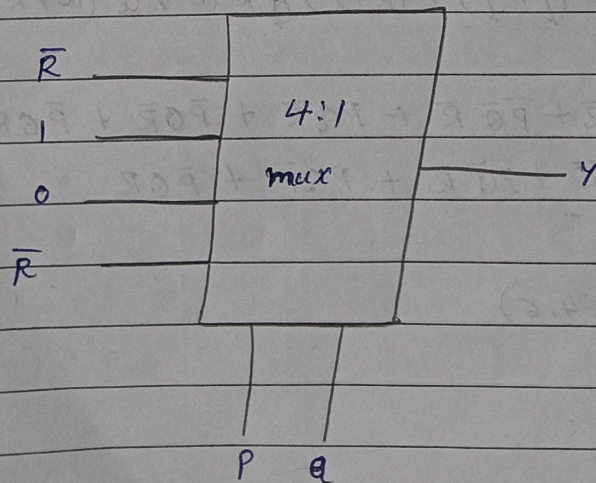

2 Implement the functionality of a full adder using 2:1 Muxes

TT of full adder

A	B	Cin	Sum	carry	A	B	Sum	carry
0	0	0	0	0	0	0	Cin	0
0	0	1	1	0	0	1	$\bar{Cin}$	Cin
0	1	0	1	0	1	0	$\bar{Cin}$	Cin
0	1	1	0	1	1	1	Cin	1
1	0	0	1	0				
1	0	1	0	1				
1	1	0	0	1				
1	1	1	1	1				

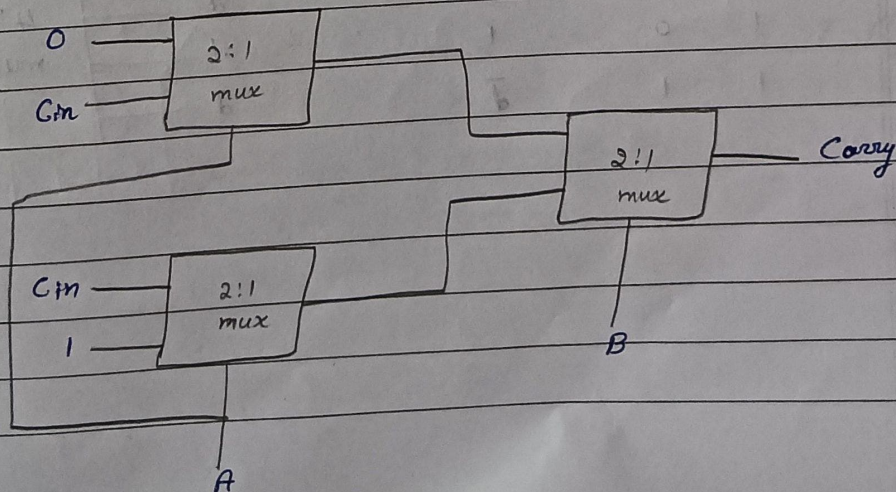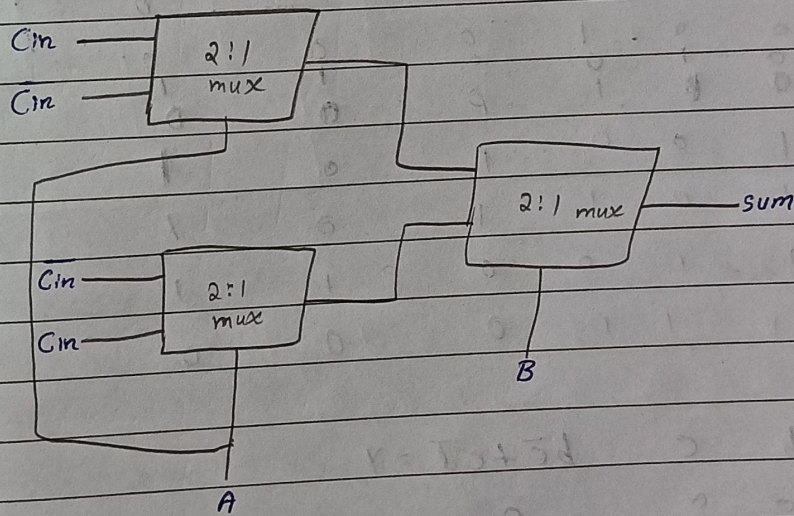

3 Simplify $f(a,b,c,d) = \sum m(2,4,5,6,10) + D(12,13,14,15)$
and implement the SOP expression using 4:1 mux

ab \ cd		cd			
		00	01	11	10
00	0	0 ₀	0 ₁	0 ₃	1 ₂
01	1	1 ₄	1 ₅	0 ₇	1 ₆
11	X	X ₁₀	X ₁₃	X ₁₅	X ₁₄
10	0	0 ₈	0 ₉	0 ₁₁	1 ₁₀

$$y = b\bar{c} + c\bar{d}$$

Let b and c be select lines

b	c	d	$b\bar{c}$	$c\bar{d}$	$b\bar{c} + c\bar{d}$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	0	0	0

b	c	$b\bar{c} + c\bar{d} = y$
0	0	0
0	1	$\bar{d}$
1	0	1
1	1	$\bar{d}$

